

ASSIGNMENT No. 6

Due Date: 22 March 2021

Frequency Response of Discretization Rules

A way to gain insight into the behaviour of different discretization rules is to look at the distortion in magnitude and phase angle introduced by the rule on the representation of a simple first-order system, such as an inductance, as a function of frequency.

1. With the rules listed below find the frequency-domain equivalent-circuit of the discretized L . Express this equivalent circuit in terms of an R_e (equivalent resistance) and an L_e (equivalent inductance). Find the simplest representation: Should R_e and L_e be in series or in parallel?
 - (a) Trapezoidal (class notes)
 - (b) Backward Euler (class notes)
 - (c) Forward Euler (derive)
 - (d) Gear's second order (derive)
2. Plot the magnitude and phase distortion of the discretizations in 1) for $f_{pu} = 0 \rightarrow 0.5$
3. Comment on the expected numerical stability based on the equivalent circuit parameters.