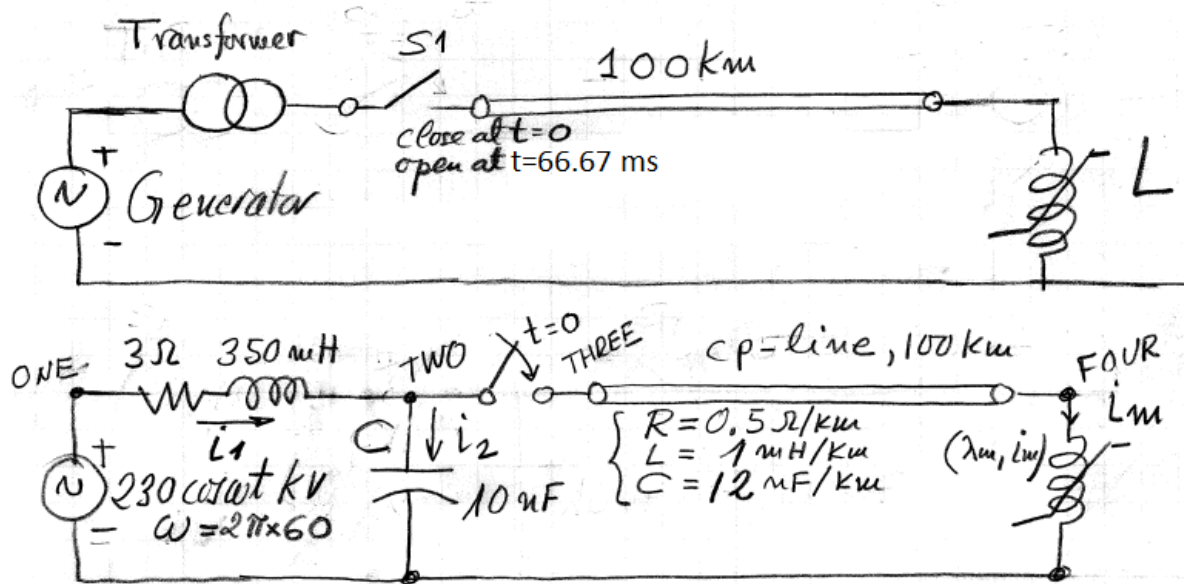


## ASSIGNMENT No. 8


Due Date: 12 April
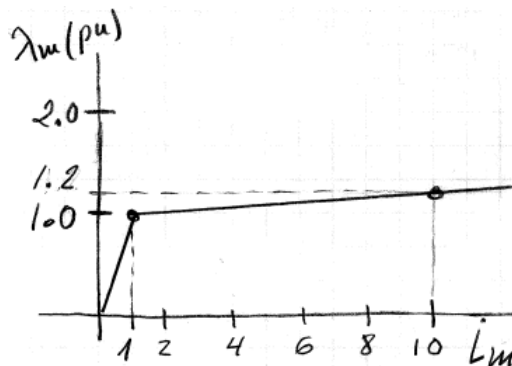
### Non-Linear Elements

The transmission line in Assignment No. 3 is now terminated in a nonlinear inductance. Adapt the program you wrote for that Assignment to the present case.



The nonlinear characteristic of the L is approximated with two line segments as follows



$\lambda_m(pu)$	$i_m(pu)$
1.0	1.0
1.2	10.0

$$\lambda_{Base} = 100 \text{ [volt.sec]}$$

$$i_{mBase} = 5 \text{ A}$$

1. Use the simple two-slope model shown. Assume zero initial conditions for both your program and PSCAD.
2. The breaker closes at  $t = 0$ . Simulate the circuit from  $t = 0$  to  $t = 200$  ms.

3. Plot  $v(one)$ ,  $v(two)$ ,  $v(three)$  on the same graph for your program and for PSCAD.
4. Plot  $i(four, ground)$  on the same graph for your program and for PSCAD.
5. Plot  $v(two, three)$  on the same graph for your program and for PSCAD.
6. Make comments comparing your results with those of PSCAD.
7. Make comments comparing your results with those of Assignment No. 3.
8. General comments.